

**Ajay Kumar Garg Engineering College, Ghaziabad**  
**Department of Electrical & Electronics Engineering**

**Model Solution ST-2**

Course: B.Tech  
 Session: 2017-18  
 Subject: Power Electronics  
 Max. Marks: 50

Semester: V  
 Section: EN1, EN2  
 Sub. Code: NEE 502  
 Time: 2 hours

**SECTION-A**

Ques: 1: Give classification of SCR commutation techniques.  
 what is load commutation?

Solution: Classification of SCR commutation techniques:

a) Line commutation or natural commutation.

b) Forced commutation

i) Load commutation or Class-A.

ii) Class-B or Resonant pulse commutation.

iii) Class-C or complementary commutation.


iv) Class-D or Impulse or Voltage Commutation.

v) External pulse commutation or Class-E.

When load elements (R, L, C) support the commutation process it is known as load commutation.

Ques: 2: Draw and label the complete protection circuit for SCR.

Solution:

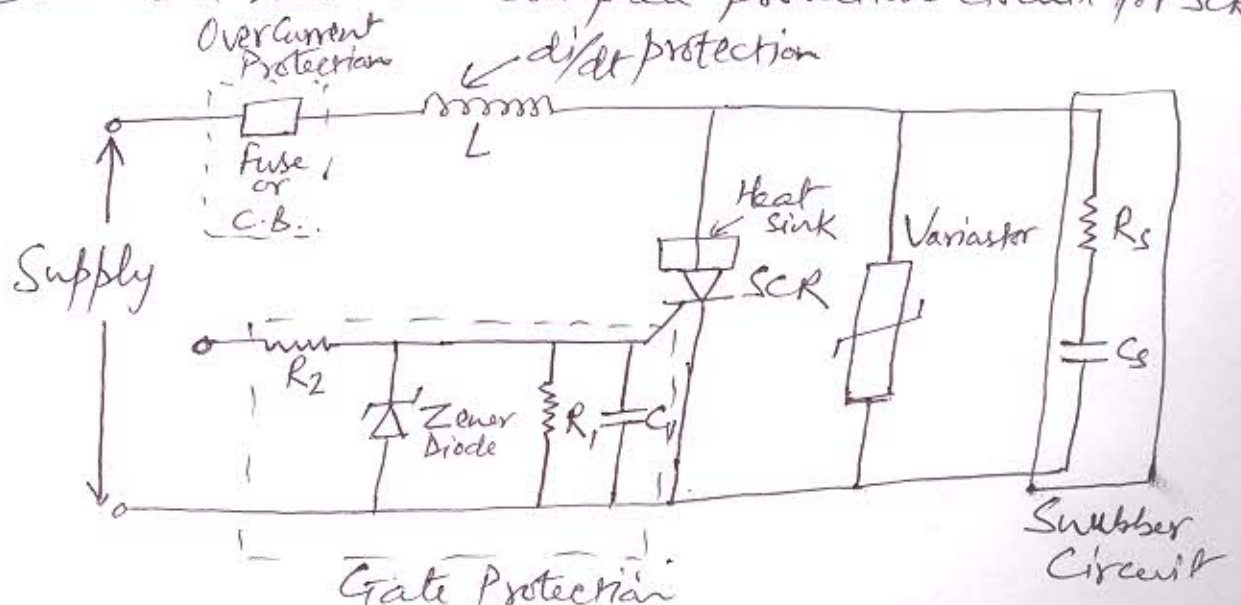

Ques: 3: Define String Efficiency for a string of series connected SCRs. why it is less than one?

Solution: String Efficiency:

$$\eta_s = \frac{\text{Total voltage across the string}}{\text{no. of SCR} \times \text{Rated voltage of SCR.}}$$

It is always less than unity due to unequal sharing of voltage/current.

Ques: 4: What do you understand by phase control in context with phase controlled converters/rectifiers?

Solution: In a circuit containing controlled, semi-conductor device/component, we can control the turn on & off duration of device and hence we can control the phase of input (AC) which will be reflected in output. Therefore we can control the portion/area of waveform to be processed.

Ques: 5: What are the advantages of using free-wheeling diode in phase controlled rectifier circuits.

Solution: Advantages of free-wheeling diode:

- It improves the input (supply) power factor.
- It improves the voltage & current waveforms.
- It reduces the voltage ripple factor.
- It improves the performance of converters.



## Section-B

Question: 6! In a power circuit four SCRs are to be connected in series. Permissible difference in their blocking voltage is 20V for a maximum difference in their blocking currents of 1mA. Difference in recovery charges is 10μC. Design suitable equalizing circuit?

Solution:

Given:

$$\Delta Q = 10 \mu C$$

$$\Delta I_b = 1 \text{ mA}$$

$$(n V_{bm} - V_s) = 20 \text{ V}$$

$$R = \frac{n V_{bm} - V_s}{(n-1) \Delta I_b} = \frac{20}{(4-1) \times 1 \times 10^{-3}}$$


$$R = 6.67 \times 10^3 \Omega = 6.67 \text{ k}\Omega$$

$$C = \frac{(n-1) \Delta Q}{n V_{bm} - V_s} = \frac{(4-1) \times 10^{-6}}{20}$$

$$C = 1.5 \times 10^{-7} = 0.15 \mu F$$


Ques: 7! With the help of relevant circuit and waveform explain class-C commutation circuit?

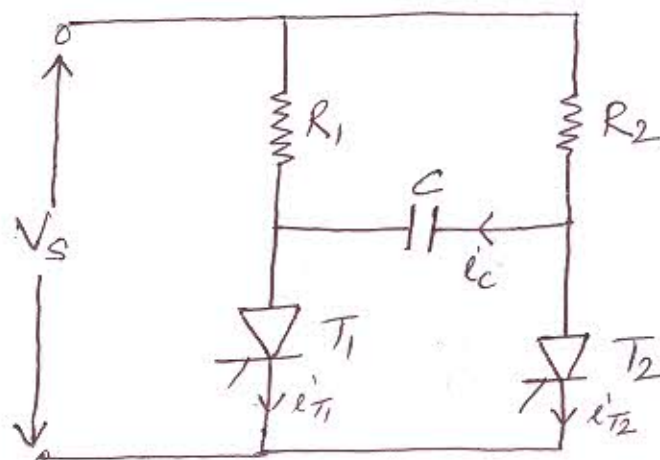Solution: Class-C or Complementary commutation!




Circuit Diagram

When  $T_1$  is ON

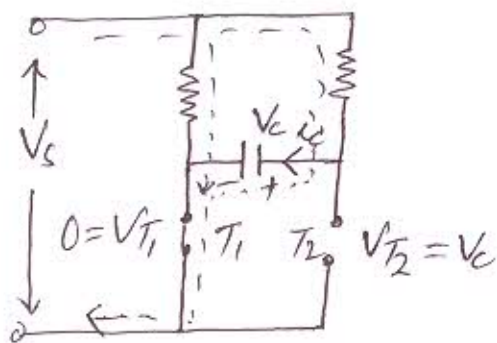


When  $T_2$  is ON

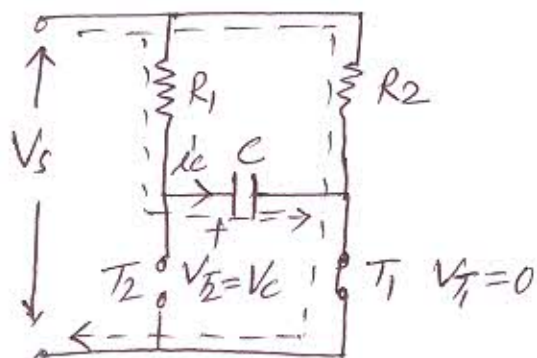

$$t_{c1} = R_1 C \ln 2$$


$$t_{c2} = R_2 C \ln 2$$

Waveform

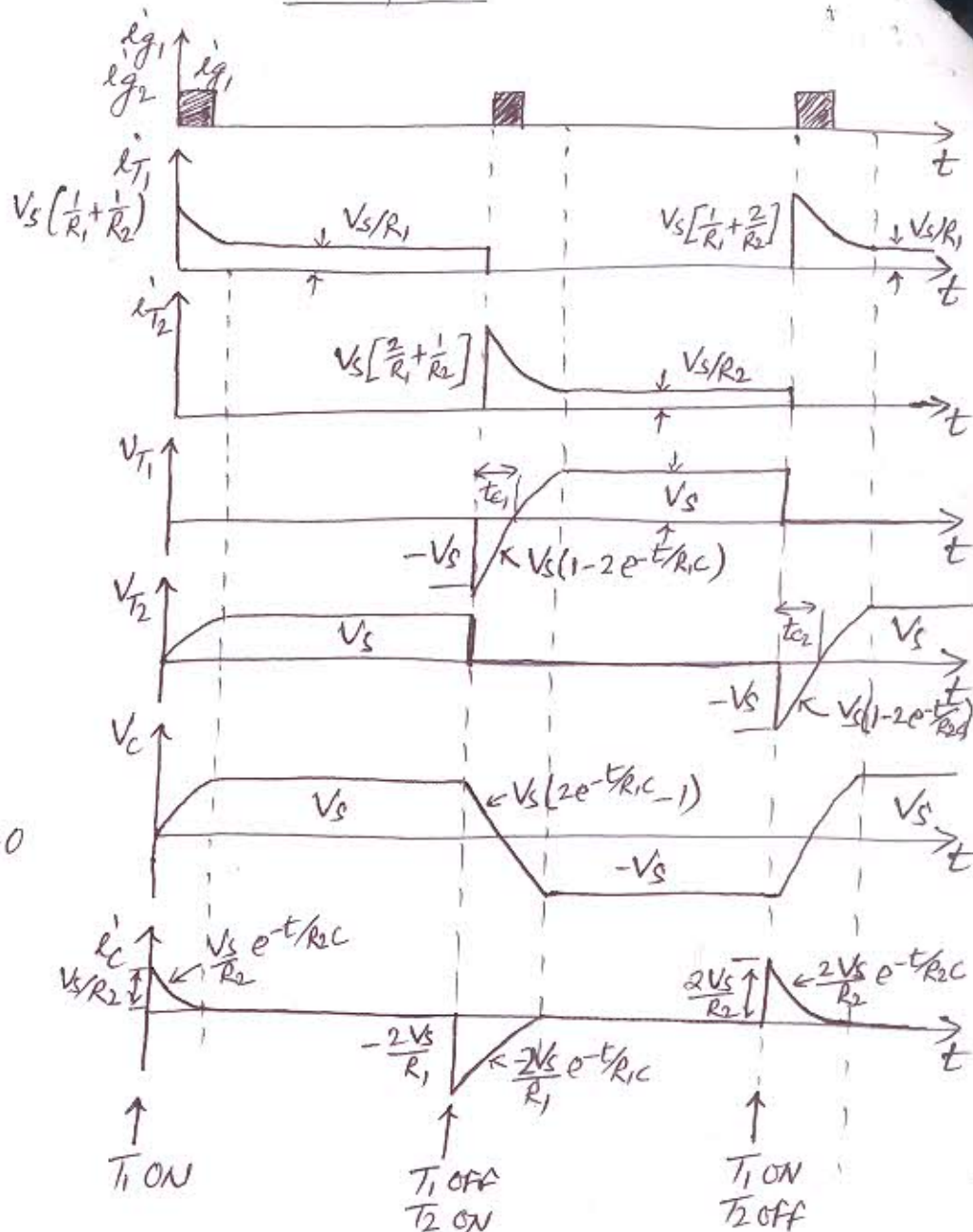

Ques: 8: A Single phase one pulse converter (SCR, controlled) is feeding an RL type of load with freewheeling diode connected across the load. Discuss the operation of circuit with help of relevant waveforms.

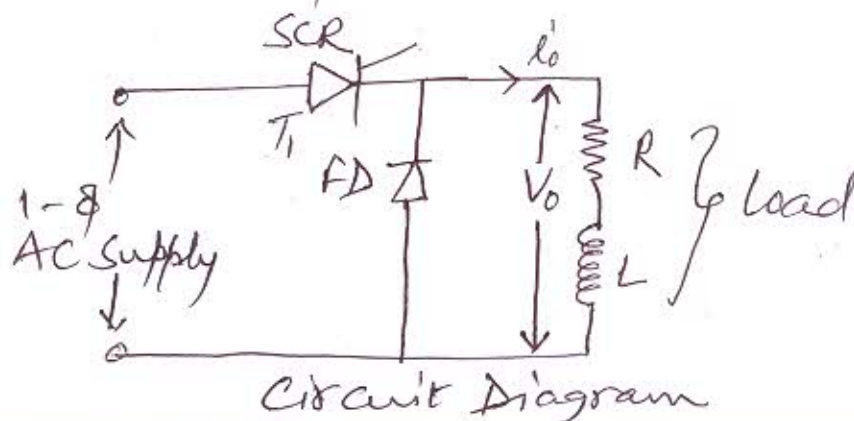Solution: 1- $\phi$  one pulse controlled SCR converter!





When  $T_1$  is triggered at  $\omega t = \alpha$  the SCR begins the conduction and it gets turned on. Inductor stores energy.

When supply voltage is reversed at  $\omega t \geq \pi$  the diode gets forward biased due to the inductor voltage reversal and SCR gets reverse biased and gets commutated.


$$V_o = \frac{1}{T} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t$$

$$= \frac{1}{2\pi} \int_{\alpha}^{\pi} V_m \sin \omega t \, d\omega t$$

$$V_o = \frac{V_m}{2\pi} (1 + \cos \alpha)$$

$$t_c = \frac{\pi}{\omega} \quad (\text{Circuit turn off time})$$

## Waveform

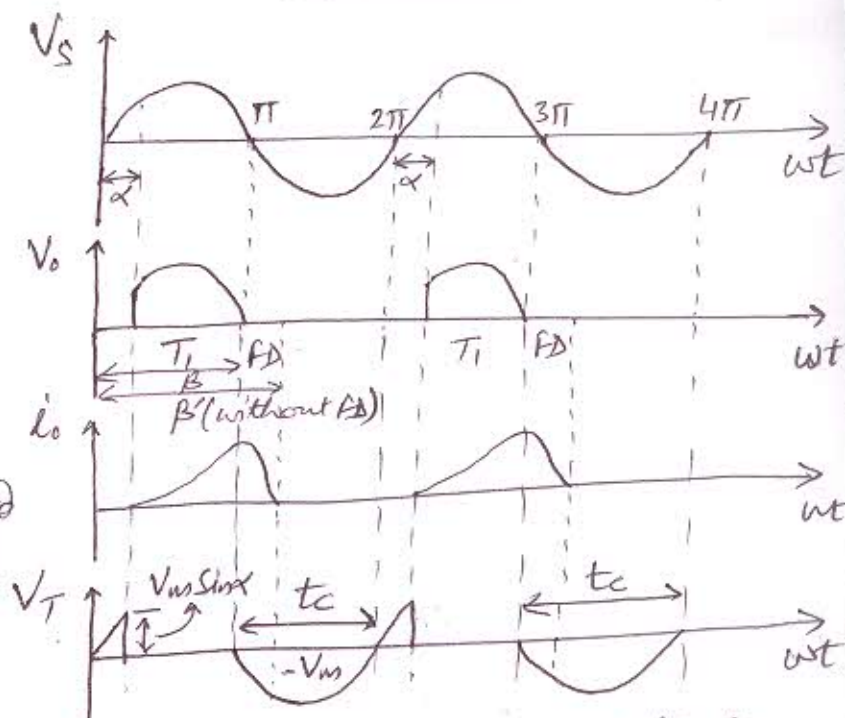

1- $\phi$  one pulse converter for RL load with free wheeling diode. Discontinuous conduction.

Ques: 9: A 1- $\phi$  full converter bridge is connected to RLE load. The source voltage is 230V, 50 Hz. The average load current of 10A is constant over the working range. For  $R = 0.4 \Omega$  and  $L = 2 \text{ mH}$  compute the firing angle delay and input power factor of converter if  $E = 120 \text{ V}$ .

Solution: Given,

$$\begin{aligned} I_o &= 10 \text{ A} \\ V_s &= 230 \text{ V} \\ R &= 0.4 \Omega \\ L &= 2 \text{ mH} \\ E &= 120 \text{ V} \end{aligned}$$

For constant load current

$$V_o = \frac{2V_m}{\pi} \cos \alpha \quad \text{and}$$

$$I_o = \frac{V_o - E}{R} \quad (V_m = 230\sqrt{2})$$

$$\therefore 10 = \frac{\frac{2\sqrt{2} \times 230}{\pi} \cos \alpha - 120}{0.4}$$



$$\therefore \cos \alpha = \frac{124 \times 3.14}{2\sqrt{2} \times 230}$$

$$\alpha = \cos^{-1}\left(\frac{124 \times 3.14}{2\sqrt{2} \times 230}\right) = 53.23^\circ$$

$$\text{Power factor} = \frac{2\sqrt{2}}{\pi} \cos \alpha = 0.5392$$

Ques: 10: With the help of relevant circuit and waveform of output voltage and output current explain the operation of a three phase half wave rectifier. Assume the firing angle delay of  $15^\circ$ .

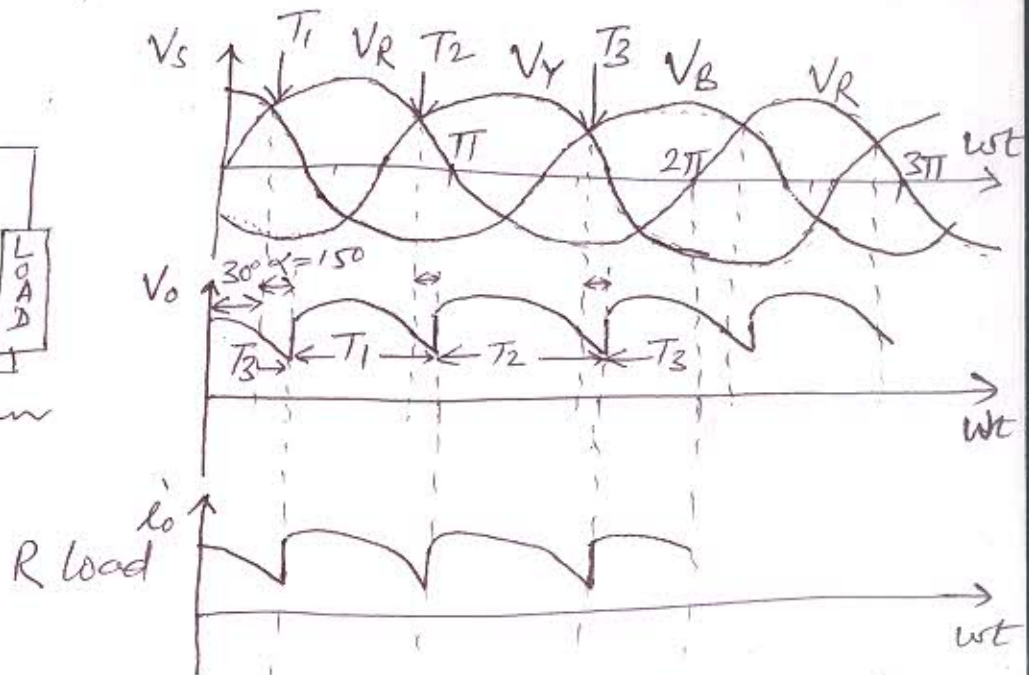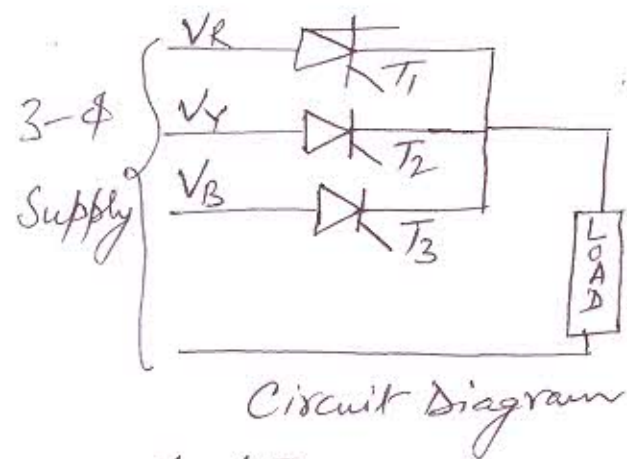Solution: 3- $\phi$  half wave rectifier:



Each thyristor conduct for  $120^\circ$ . when firing angle  $\alpha < 30^\circ$  continuous conduction is obtained.

Continuous Conduction for 3- $\phi$  Half wave Rectifier

$$V_o = \frac{1}{2\pi} \int_{\frac{\pi}{6} + \alpha}^{\frac{5\pi}{6} + \alpha} V_{mp} \sin \omega t d\omega t$$


$$V_o = \frac{3\sqrt{3} V_{mp}}{2\pi} \cos \alpha = \frac{3 V_{mL}}{2\pi} \cos \alpha$$




## Section-C

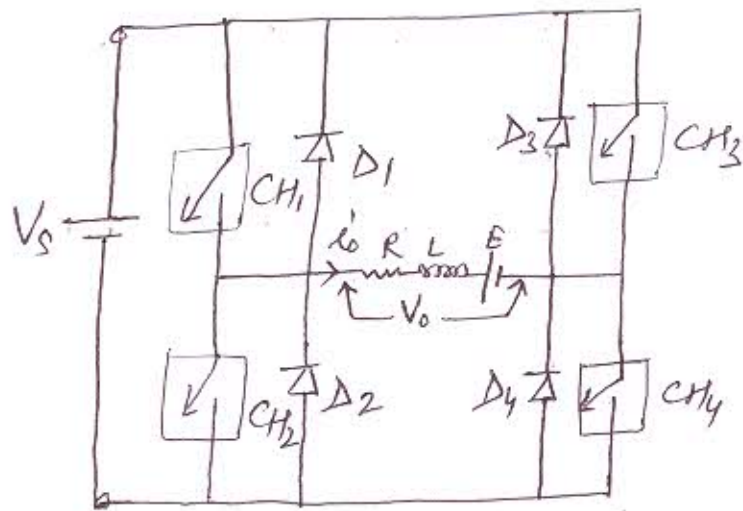Question: 11: Describe the operation of E-type chopper with relevant circuit diagrams and its operation in all the four quadrants?

Solution: Type-E chopper: (Four quadrant operation)



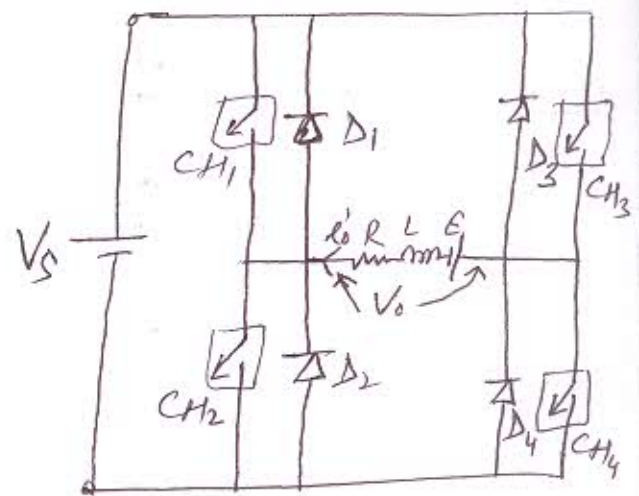① I<sup>st</sup> & II<sup>nd</sup> quadrant operation



② III<sup>rd</sup> and IV<sup>th</sup> quadrant operation

Circuit Diagram

CH<sub>2</sub> operated, CH<sub>1</sub>, CH<sub>3</sub> & CH<sub>4</sub> kept off  
CH<sub>2</sub> - on  $i_o$  is negative.

L stores energy hence  $(E + L \frac{di_o}{dt}) > V_s$

CH<sub>2</sub> - off now  $i_o$  flow from load to source through D<sub>1</sub> D<sub>4</sub>.

CH<sub>2</sub> on step-up mode.

Power flow from load to source

$V_o$  is positive and  $i_o$  is negative

therefore regenerative braking.

2<sup>nd</sup> quadrant (fig: a circuit diagram)

CH<sub>1</sub> kept off, CH<sub>2</sub> kept on & CH<sub>3</sub> operated  
polarity of E must be reversed (fig: b)

CH<sub>3</sub> - on load is connected to  $V_s$

therefore  $V_o$  &  $i_o$  are negative

CH<sub>3</sub> - off negative  $i_o$  free wheels through D<sub>4</sub> CH<sub>2</sub>

2 choppers on step down mode.

Power flow from source to load.

Reverse motoring mode.

3<sup>rd</sup> quadrant operation.

CH<sub>4</sub> is kept on, CH<sub>3</sub> kept off, CH<sub>1</sub> is operated  
2 choppers are on step down

CH<sub>1</sub> - CH<sub>4</sub> on

CH<sub>1</sub> turn off then CH<sub>4</sub> - D<sub>2</sub> conduct

$V_o$  &  $i_o$  are positive

Power flow from source to load hence

Forward motoring mode

1<sup>st</sup> quadrant operation.

Fig: a. Circuit diagram

CH<sub>4</sub> is operated & other choppers are kept off.

CH<sub>4</sub> - on  $i_o$  flow through CH<sub>4</sub> D<sub>2</sub> L & E.

L stores energy

CH<sub>4</sub> - off  $i_o$  flow from load to source through D<sub>2</sub> D<sub>3</sub>.

$V_o$  is negative and  $i_o$  is positive.

Power flow from load to source.

1 chopper on step-up mode.


Braking mode.

4<sup>th</sup> quadrant operation (fig: b).



Ques: 12: A single phase controlled converter is feeding RLE type of load. With the help of relevant circuit and the waveforms explain its operation in rectification mode. Also derive the equation for average output voltage.

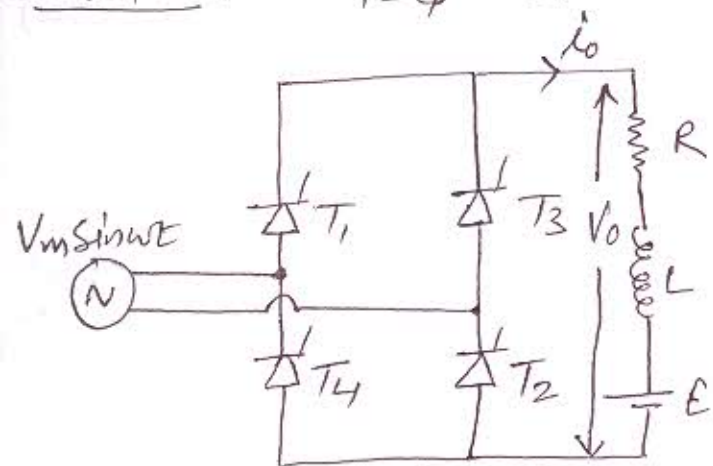Solution: 1- $\phi$  converter feeding RLE load.



Circuit Diagram

This circuit contains four thyristors divided in two groups.

$T_1 T_2$  conduction occurs when supply voltage waveform is positive and  $T_3 T_4$  conducts for negative supply waveform.

For positive supply voltage  $T_1 T_2$  are forward biased and  $T_1 T_2$  can be triggered if  $V_s \geq E$  therefore minimum firing angle could be in between  $0$  &  $0_2$ .


$$\alpha_{\min} = 0, \quad \alpha_{\max} = 0_2. \quad (\text{at } 0_1, V_m \sin 0_1 = E; \text{ at } 0_2, V_m \sin 0_2 = E)$$

In the rectification mode  $\alpha$  should not exceed the  $wt = 90^\circ$  so that output voltage is positive. therefore firing angle is restricted to max  $90^\circ$ .

For negative supply voltage  $T_3 T_4$  are triggered and outgoing SCR ( $T_1 T_2$ ) get commutated and  $T_3 T_4$  (incoming group of SCR) are turned on.

$$\text{Output average voltage } V_o = \frac{1}{\pi} \int_{\alpha}^{\pi+\alpha} V_m \sin wt \, dwt$$

$$V_o = \frac{2V_m}{\pi} \cos \alpha.$$

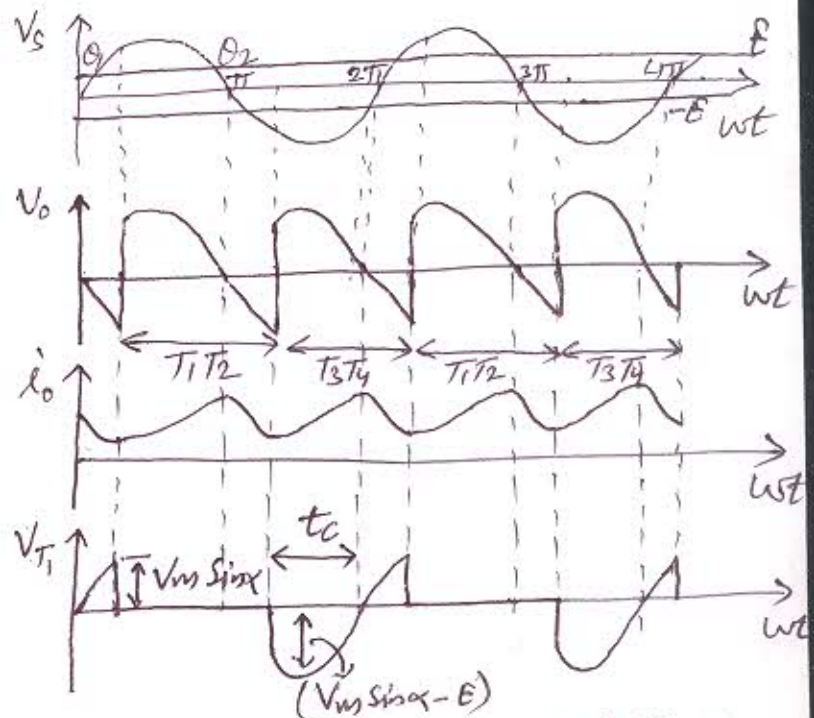

Waveform for 1- $\phi$  full wave RLE load converter in continuous conduction