

AJAY KUMAR GARG ENGINEERING COLLEGE, GHAZIABAD**DEPARTMENT OF ELECTRICAL & ELECTRONICS ENGG.****SESSIONAL TEST - 2**

Course : B. Tech.
Session : 2017-18
Subject : EMMI
Max. Marks : 50

Semester : III
Section : EN- 1 & 2
Sub. Code : REE-302
Time : 2 hours

Note: Answer **all** the sections

Section A

A. Attempt all the parts.

(5x2=10)

1. Give the range for measurement of low, medium and high resistance. L
2. Justify unsuitability of Hay's Bridge for measurement of low Q inductor. M
3. Why the secondary of C.T. should never be open while the primary winding is energized? L
4. Define burden of instrument transformers. L
5. What is the use of guard circuit in the measurement of high resistance? L

Section B

B. Attempt all the parts.

(5x5=25)

6. Derive balance equation of Anderson's Bridge along with its phasor diagram. Mention advantages and disadvantages of this bridge. H
7. A 100/5 A, 50 Hz current transformer has a bar primary and a rated secondary burden of 12.5 VA. The secondary winding has 196 turn and a leakage reactance of 0.96mH. with a purely resistive at full rated load, the magnetization mmf is 16 A and the loss excitation requires 12 A. Find the ratio and phase angle error. M
8. Describe Voltmeter-Ammeter method for the measurement of medium resistance. L

9. Explain the measurement of low resistance using Kelvin's Double Bridge. Derive the condition for balance.
10. A single phase potential transformer has a turn ratio of 3810/63. The nominal secondary voltage is 63 V and total equivalent resistance and leakage reactance referred to the secondary side are 2Ω and 1Ω respectively. Calculate the ratio and phase angle errors when the transformer is supplying a burden of $100 + j200 \Omega$. State the assumptions made.

Section C

C. Attempt all the parts.

(7.5x2=15)

11. Derive the expression for ratio and phase angle error in case of current transformer.
12. Discuss the following methods for high resistance measurement:
- Loss of charge method.
 - Megohm Bridge.

$$I_s = \frac{63}{(102)^2 + (200)^2} = 0.239 \text{ A}$$

$$\eta = \frac{I_s \cos \phi}{V} = \frac{0.239 \cos 60.5^\circ}{63}$$

$$\eta = 0.49 \text{ or } 49\%$$

$$\frac{60 - 60.98}{60.98} = -0.78\%$$