

Ajay Kumar Garg Engineering College, Ghaziabad

Department of Electrical & Electronics Eggs.

SESSIONAL TEST-2

Course: B. Tech.
 Session: 2017-18 Odd
 Subject: Network Analysis & Synthesis
 Max. Marks: 50

Semester: III
 Section: EC-1, EC-2, EC-3 & EI
 Sub. Code: REE-305
 Time Allowed: 2 Hours

Section-A

A. Attempt all parts.

(5x2 = 10)


1. Define Laplace Transform and distinguish between one-sided two-sided Laplace Transforms. M
2. Define Initial value and final value theorems. H
3. Define the terms Planar Graph and tree. L
4. What do you mean by duality in an electric network? L
5. What is Bode plot? H

Section-B

B. Attempt all parts.

(5x5=25)

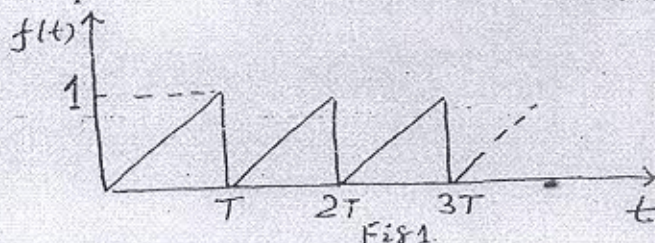6. Prove that signals $x_1(t) = e^{-at} u(t)$ and $x_2 = -e^{-at} u(-t)$ have the same Laplace Transform but differ in Region of Convergence (ROC). Plot also their ROCs. L
7. Find the Laplace Transform of the Periodic Waveform shown in Fig.1 H




8. Draw the pole-zero plot of the network function M

$$F(s) = \frac{3s}{(s+1)(s+4)}$$

And obtain the $f(t)$ from pole-zero plot.

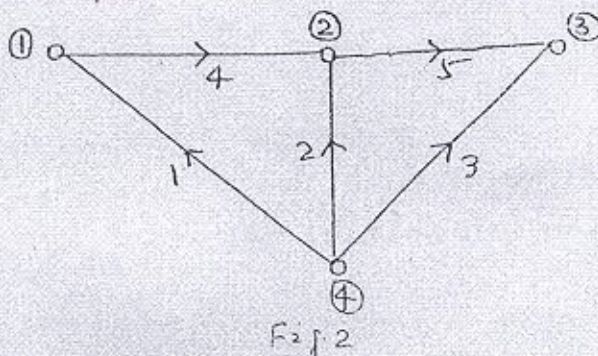9. For the graph shown in Fig 2, obtain the basic loop matrix and basic cut-set matrix. Take 1, 2 and 3 as tree branches. M



10. State the Routh-Hurwitz stability criteria. Using Routh stability criteria, check the stability of the system whose characteristic equation is given by M
 $q(s) = 2s^5 + s^4 + 6s^3 + 3s^2 + s + 1$

Section- C

C. Attempt all parts.

(2x7.5=15)

11. State the Superposition theorem. Using Thevenin's theorem find the current through the capacitor for the circuit shown in Fig. 3 H

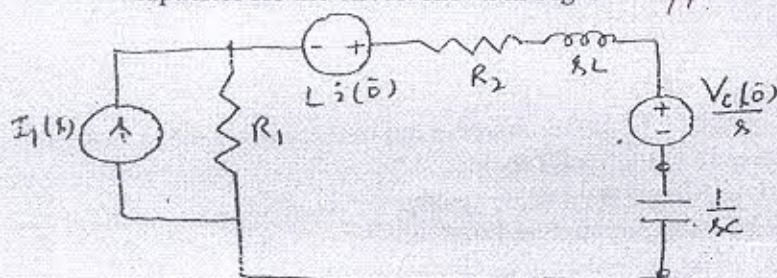


Fig. 3

12. Using graph theory, obtain the node equations of the network shown in Fig. 4 M

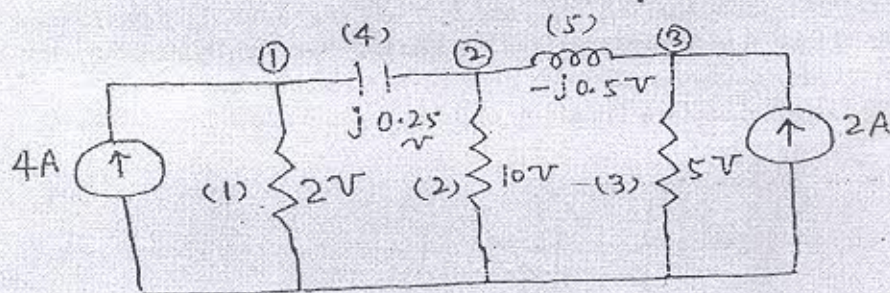


Fig. 4
